

ELEC 4700

Assignment 4

Circuit Modeling

Liam Anderson
100941879
April 5 2020

1. and 2.

```
% My assignment 3 was terrible...
% But if I had the IV data from A3 I would
% find the linear fit and R3 like this:
```

```
poly = polyfit(v, i, 1);
fit = poly(1)*v + poly(2);
R3 = poly(1)
```

3.

a.

Eq's

- ① $\frac{1}{R_1} (V_1 - V_2) + i_{in} = 0$
- ② $\frac{1}{R_1} (V_2 - V_1) + \frac{V_2}{R_2} = 0$
- ③ $\frac{V_3}{R_3} - i_L = 0$
- ④ $\frac{1}{R_4} (V_4 - V_5) + i_3 = 0$
- ⑤ $\frac{1}{R_4} (V_4 - V_5) + \frac{V_5}{R_6} = 0$
- ⑥ $V_1 = [-10:10] \text{ SWEEP} \rightarrow \text{in space}$
- ⑦ $V_2 - V_3$
- ⑧ $-\frac{2V_3}{R_3}$

7+1 nodes

	1	2	3	4	5	i_{in}	i_L	i_3
1	$1/R_1$	$-1/R_1$	0	0	0	1	0	0
2	$-1/R_1$	$1/R_1 + 1/R_2$	0	0	0	0	1	0
3	0	0	$1/R_3$	0	0	0	-1	0
4	0	0	0	$1/R_4 + 1/R_6$	$-1/R_6$	0	0	1
5	0	0	0	$-1/R_4$	$1/R_6$	0	0	0
6	1	0	0	0	0	0	0	0
7	0	1	-1	0	0	0	0	0
8	0	0	$-2/R_3$	1	0	0	0	0

Voltages
↑
currents

Note: See appendix for finite difference derivations

$$C = \begin{bmatrix} 1 & 2 & 3 & 4 & 5 & 6 & 7 & 8 \\ C & -C & 0 & 0 & 0 & 0 & & \\ 2 & -C & C & 0 & & & & \\ 3 & 0 & 0 & 0 & & & & \\ 4 & & & & & & & \\ 5 & & & & & & & \\ 6 & & & & & & & \\ 7 & & & & & & & \\ 8 & & & & & & & \end{bmatrix}$$

etc.


0's

$$G = \begin{bmatrix} 1.0000 & -1.0000 & 0 & 0 & 0 & 0 & 0 & 1.0000 \\ -1.0000 & 1.5000 & 0 & 0 & 0 & 1.0000 & 0 & 0 \\ 0 & 0 & 0.1000 & 0 & 0 & -1.0000 & 0 & 0 \\ 0 & 0 & 0 & 10.0000 & -10.0000 & 0 & 1.0000 & 0 \\ 0 & 0 & 0 & -10.0000 & 10.0010 & 0 & 0 & 0 \\ 0 & 1.0000 & -1.0000 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & -10.0000 & 1.0000 & 0 & 0 & 0 & 0 \\ 1.0000 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \end{bmatrix};$$


$$C = \begin{bmatrix} \text{Cap} & -\text{Cap} & 0 & 0 & 0 & 0 & 0 & 0 \\ -\text{Cap} & \text{Cap} & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & -L & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \end{bmatrix};$$


$$F = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 1 \end{bmatrix};$$

b.

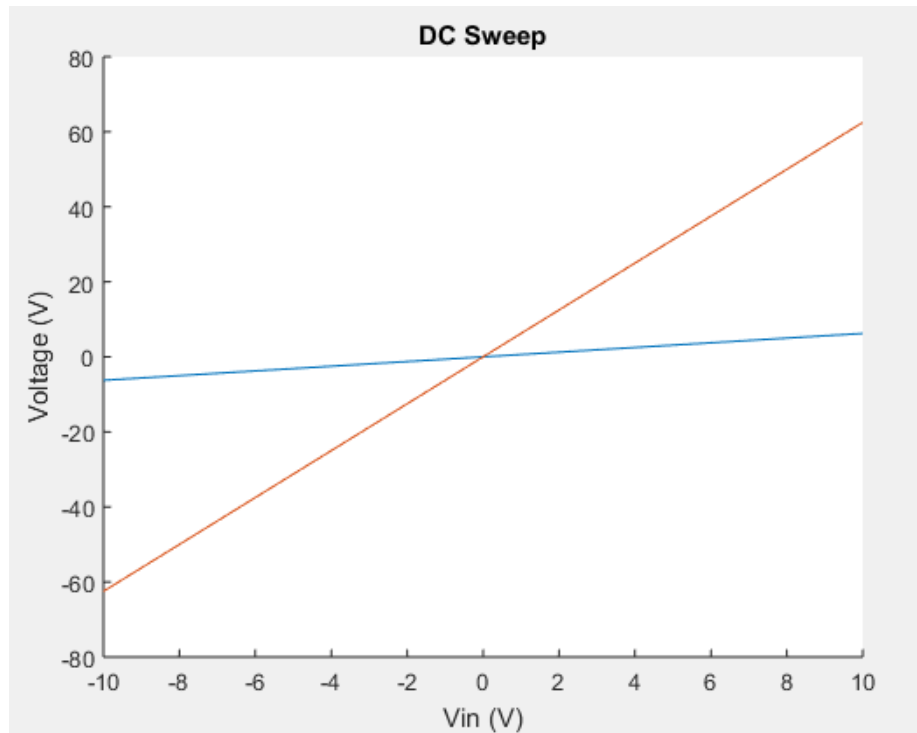

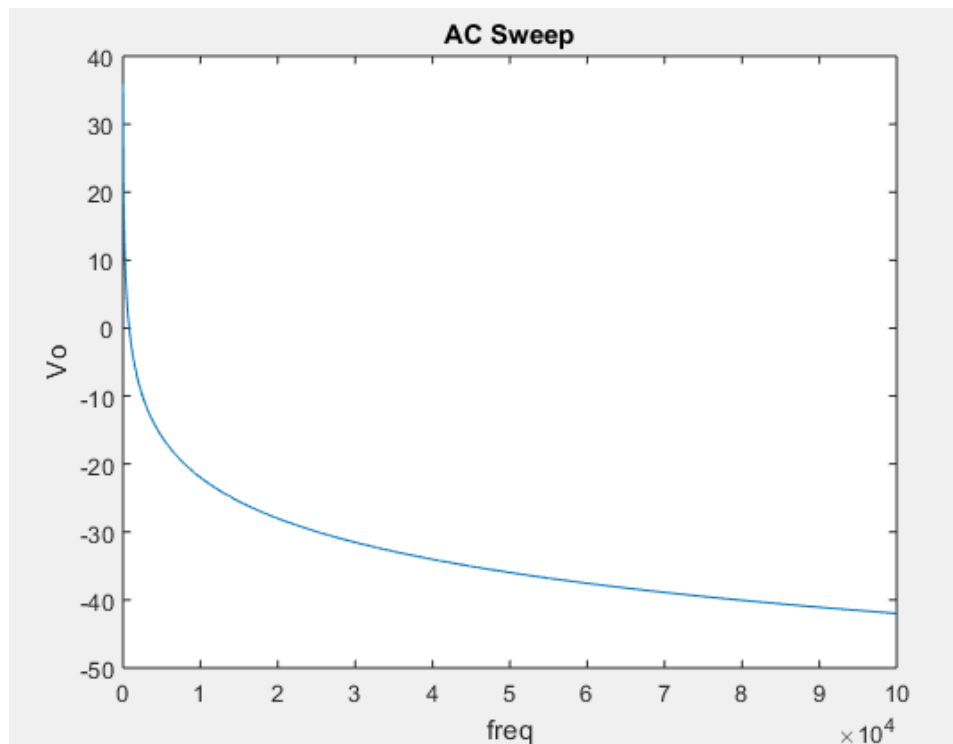* For DC above, note that the blue line is V1 and the orange line is Vout



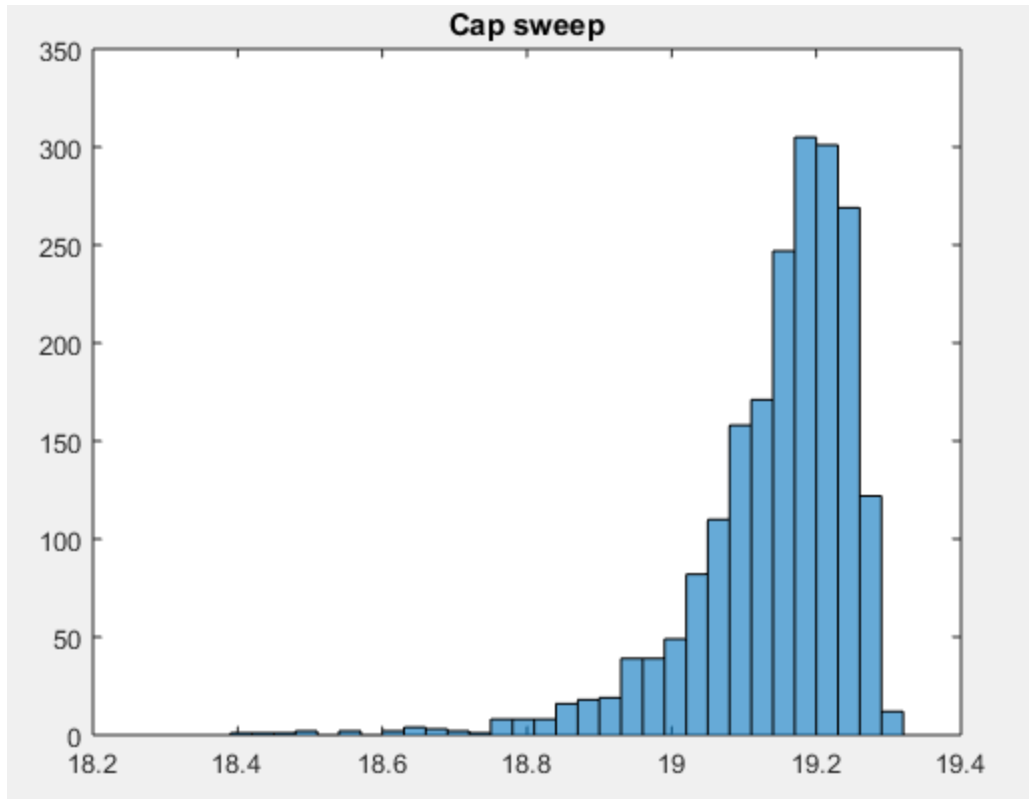



4.



a. This circuit is a low-pass filter. This is proven by the AC Sweep graph. It is also predictable, given the presence of the inductor.



b. If it behaves like a normal filter, then it would have a high gain at low frequencies, up to the chosen cut-off frequency where it should drop by 3dB and then begin to drop sharply, again how sharp is dependent on the design.



c. See appendix for finite difference derivations

d.

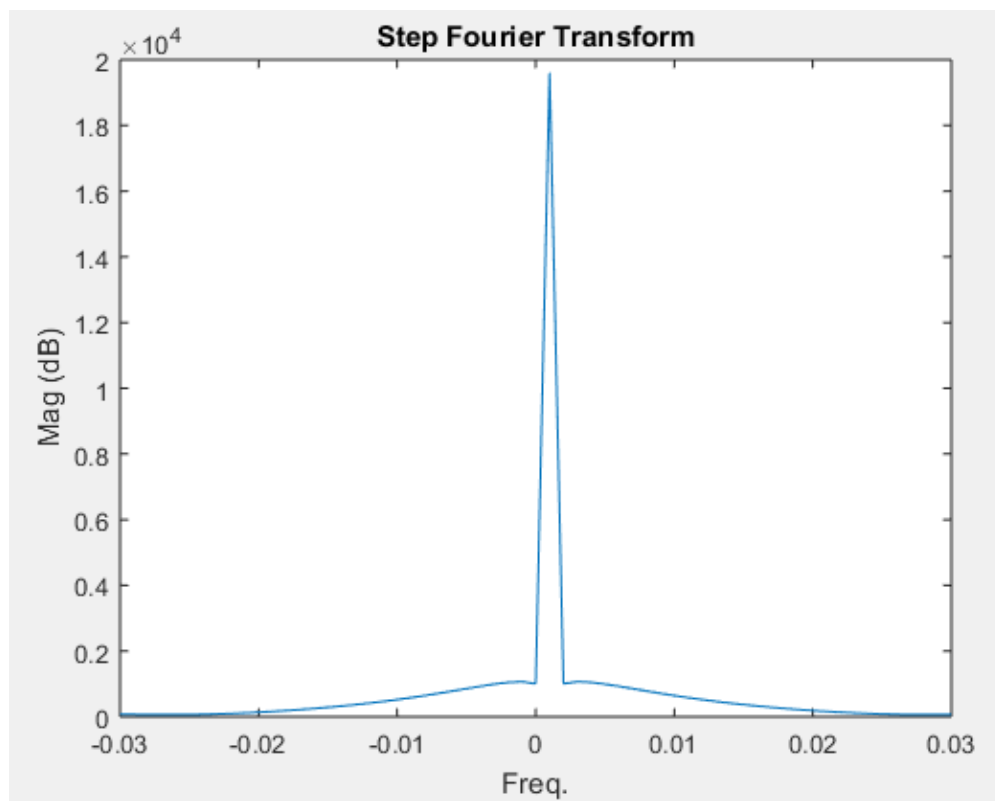
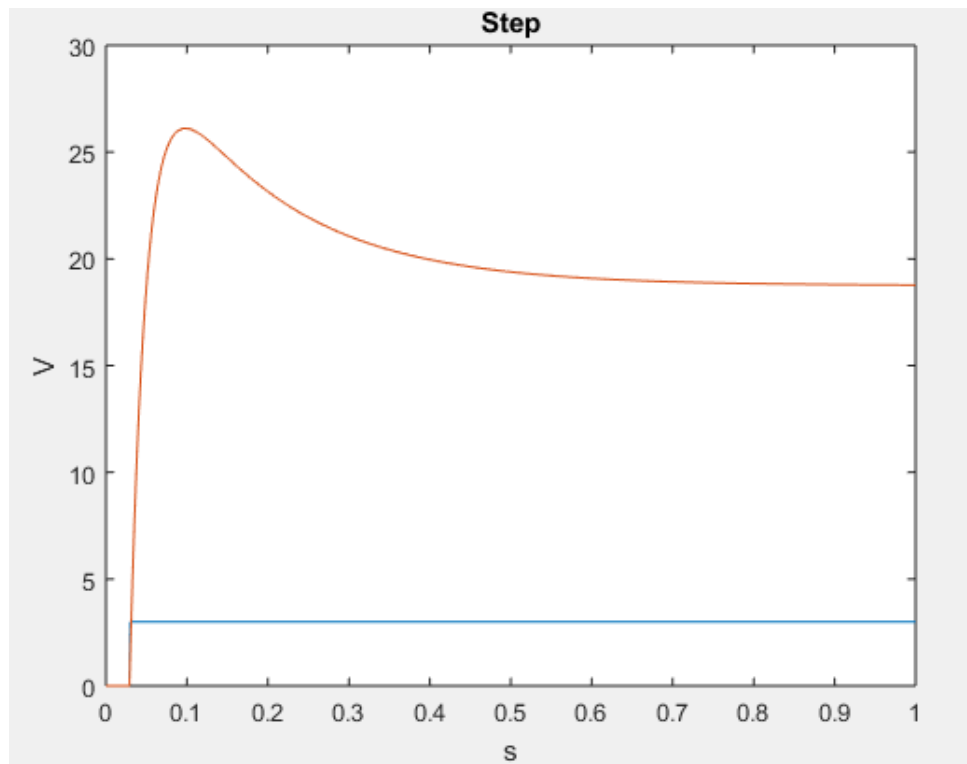


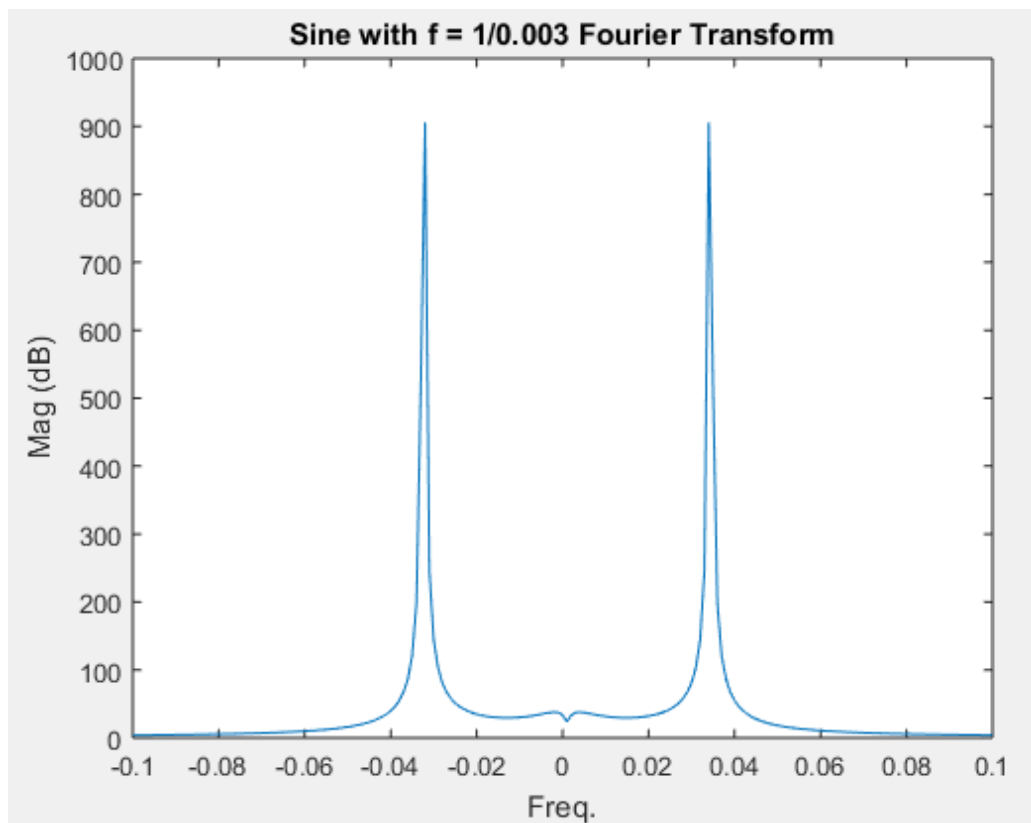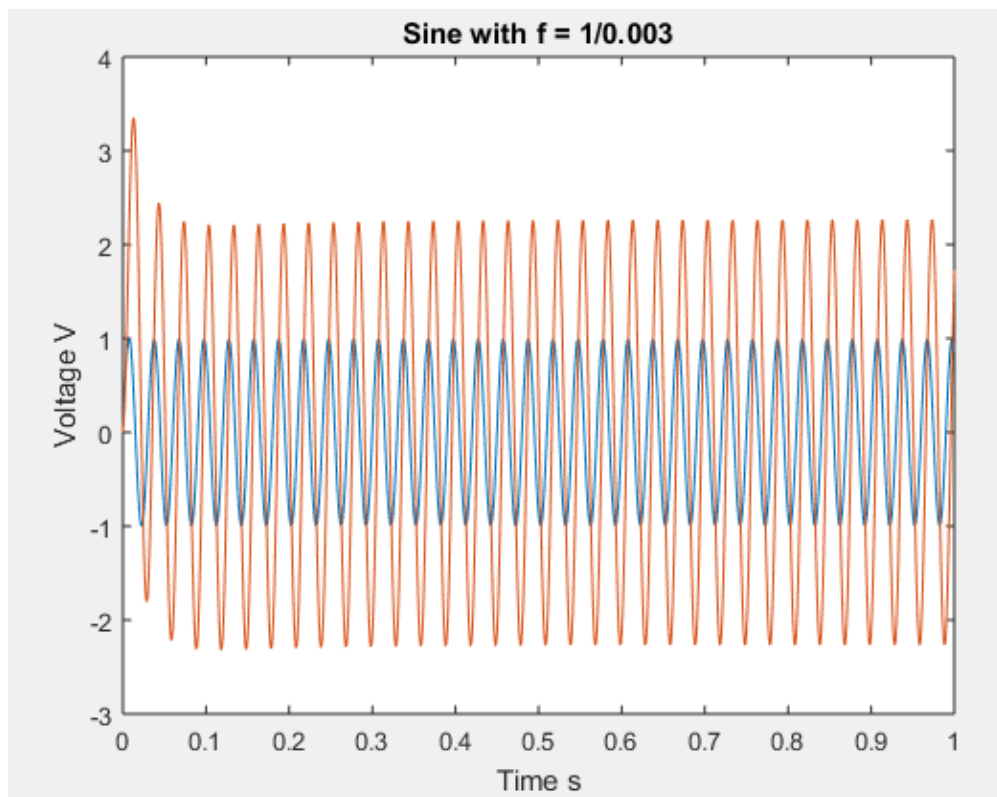

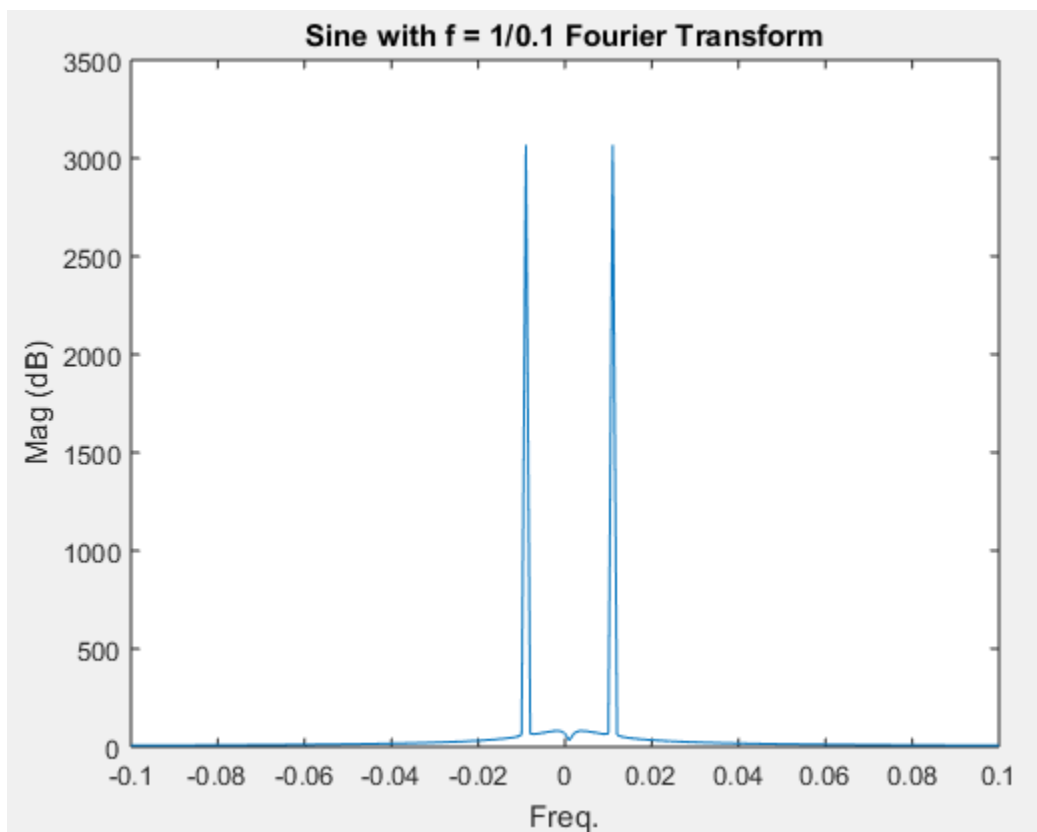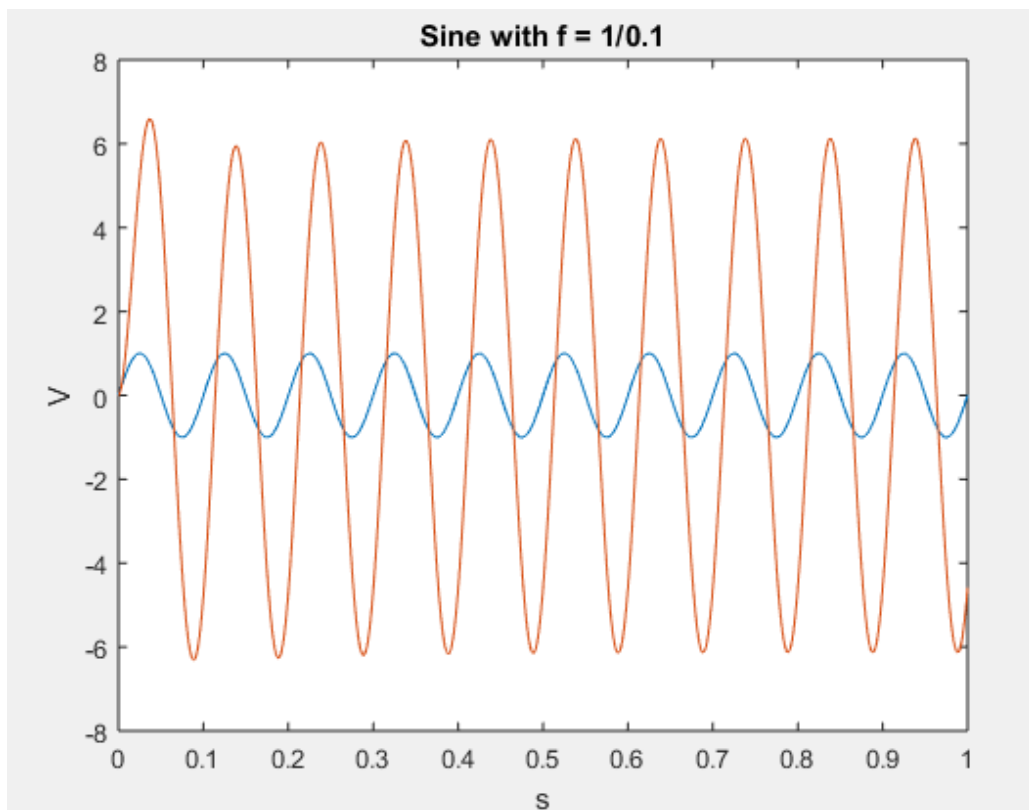

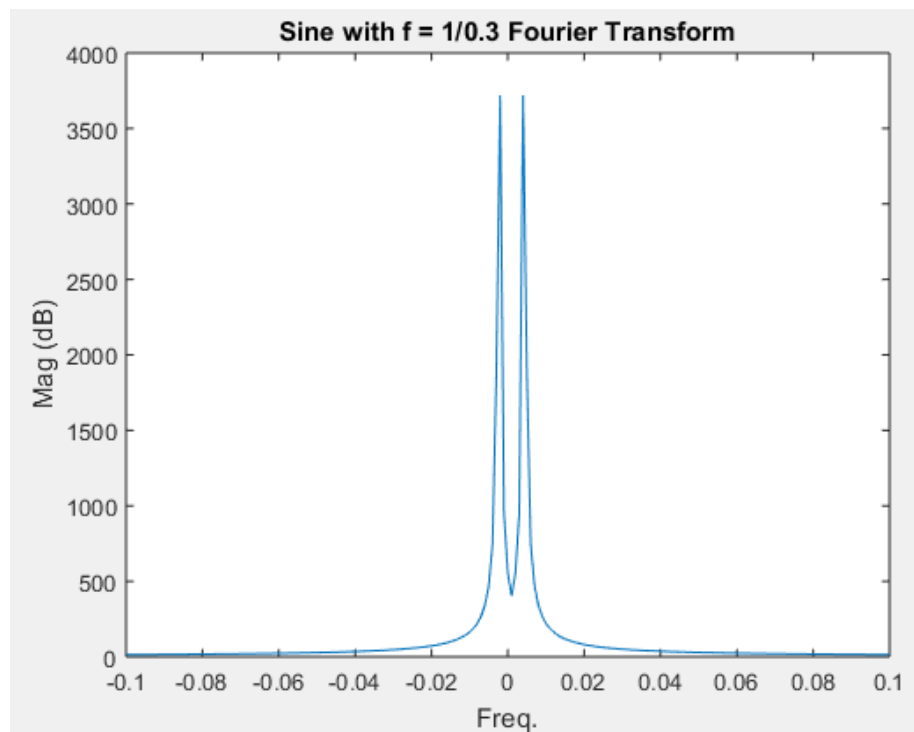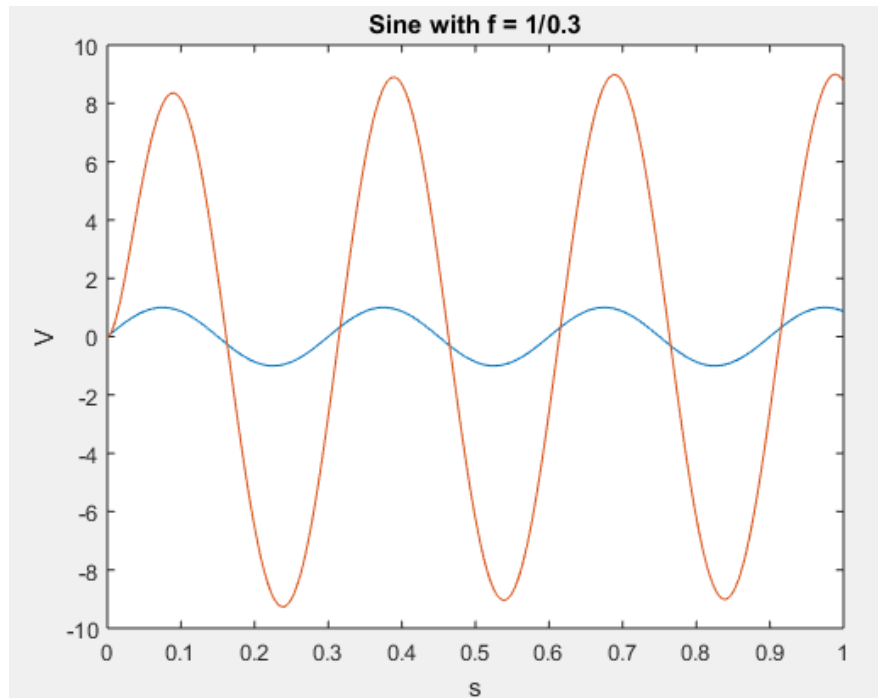

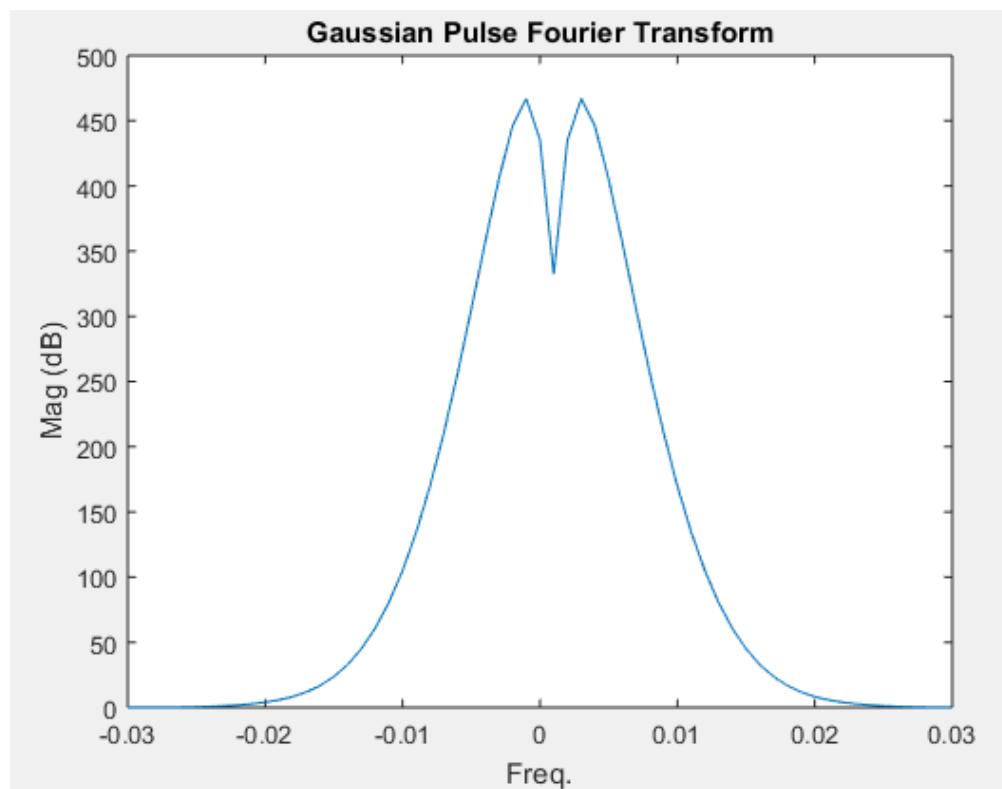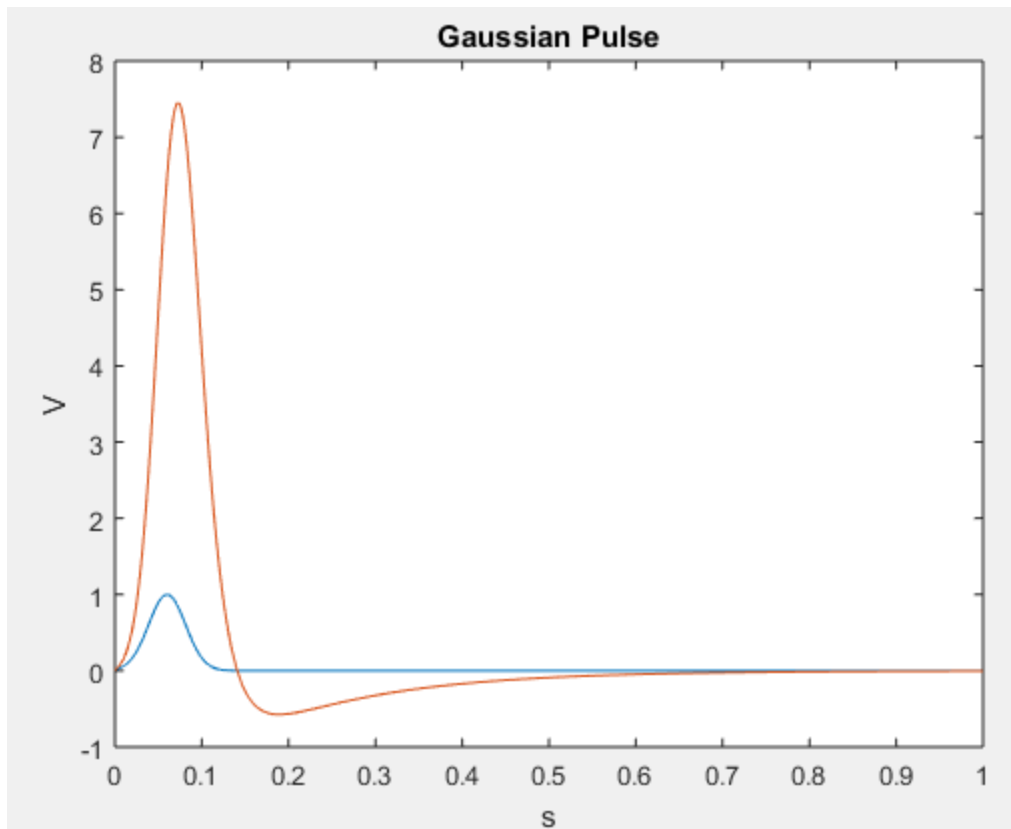
- It appears that as the frequency is decreased (slowed down), the gain increases. It can be assumed that the opposite would be true for increasing frequency.






Decreasing the timestep will make the simulation more detailed (see Q5)


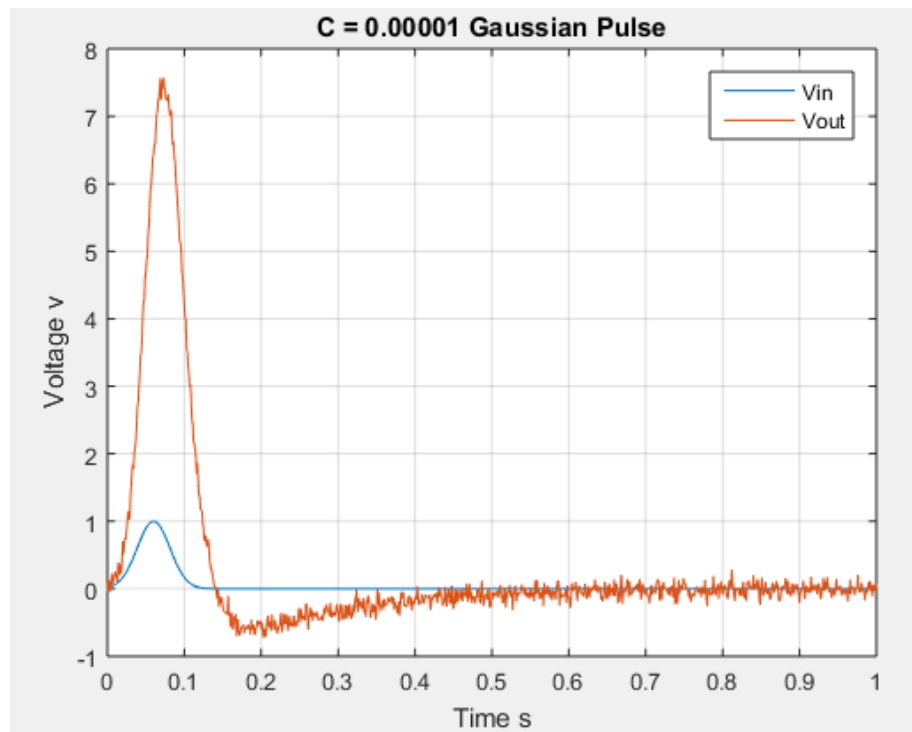
5.



```
C = [
    Cap    -Cap    0    0    0    0    0    0    0    ;
   -Cap    Cap    0    0    0    0    0    0    0    ;
    0      0    Cnew  0    0    0    0    0    0    ;
    0      0    0    0    0    0    0    0    0    ;
    0      0    0    0    0    0    0    0    0    ;
    0      0    0    0    0    -L    0    0    0    ;
    0      0    0    0    0    0    0    0    0    ;
    0      0    0    0    0    0    0    0    0    ;
    1;
];
```




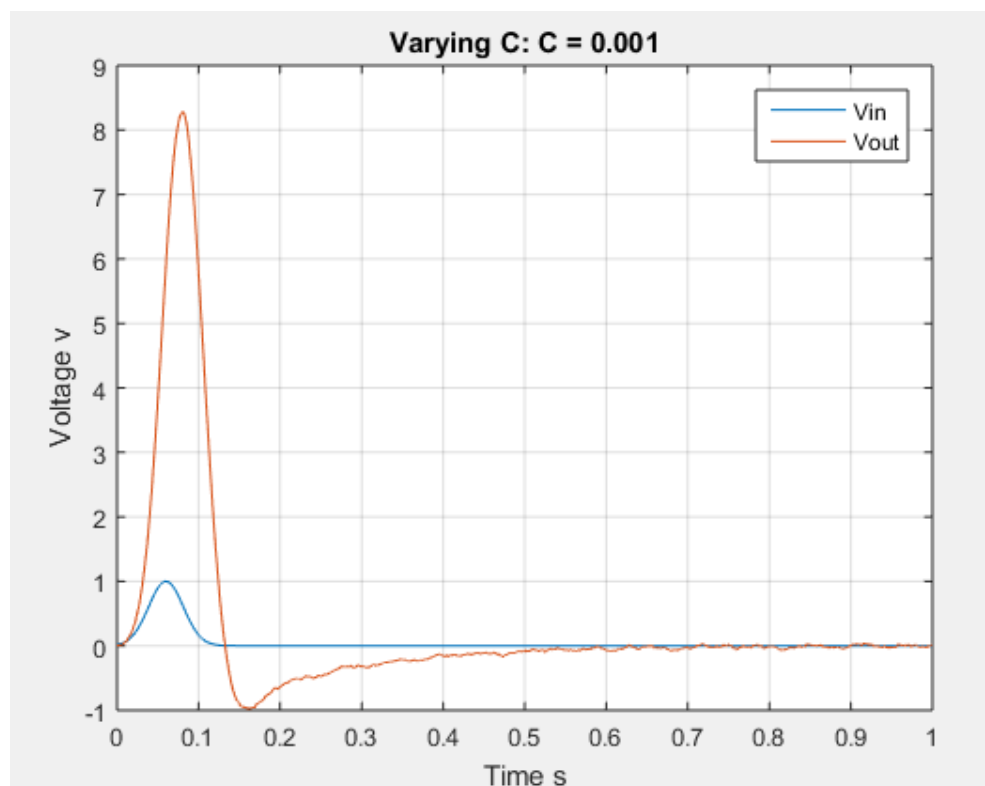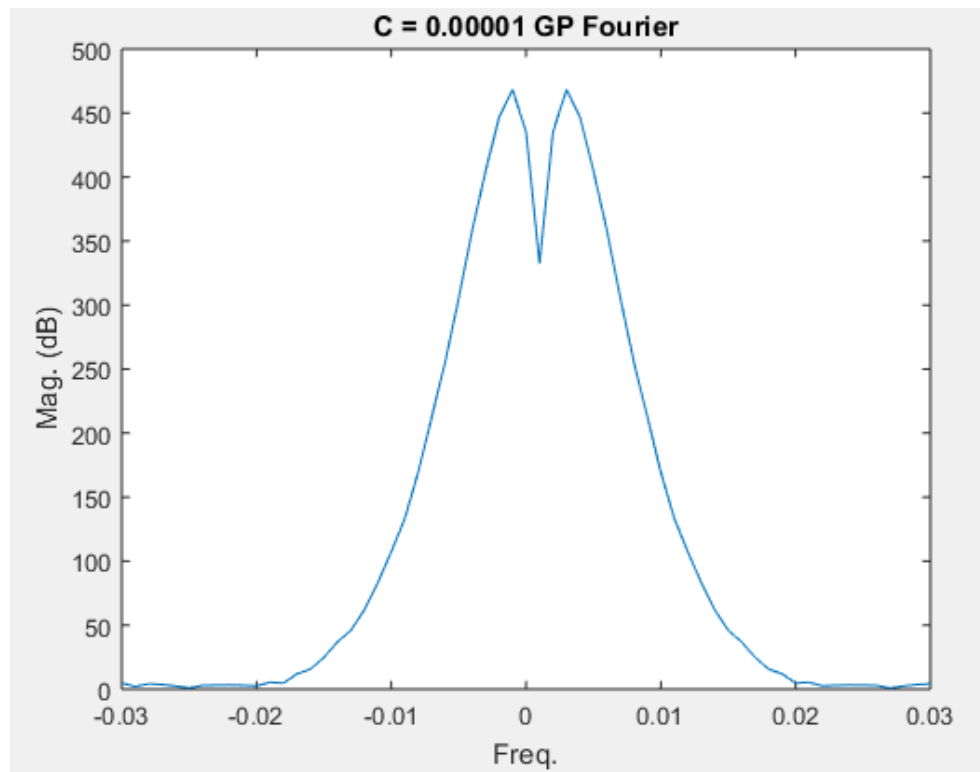

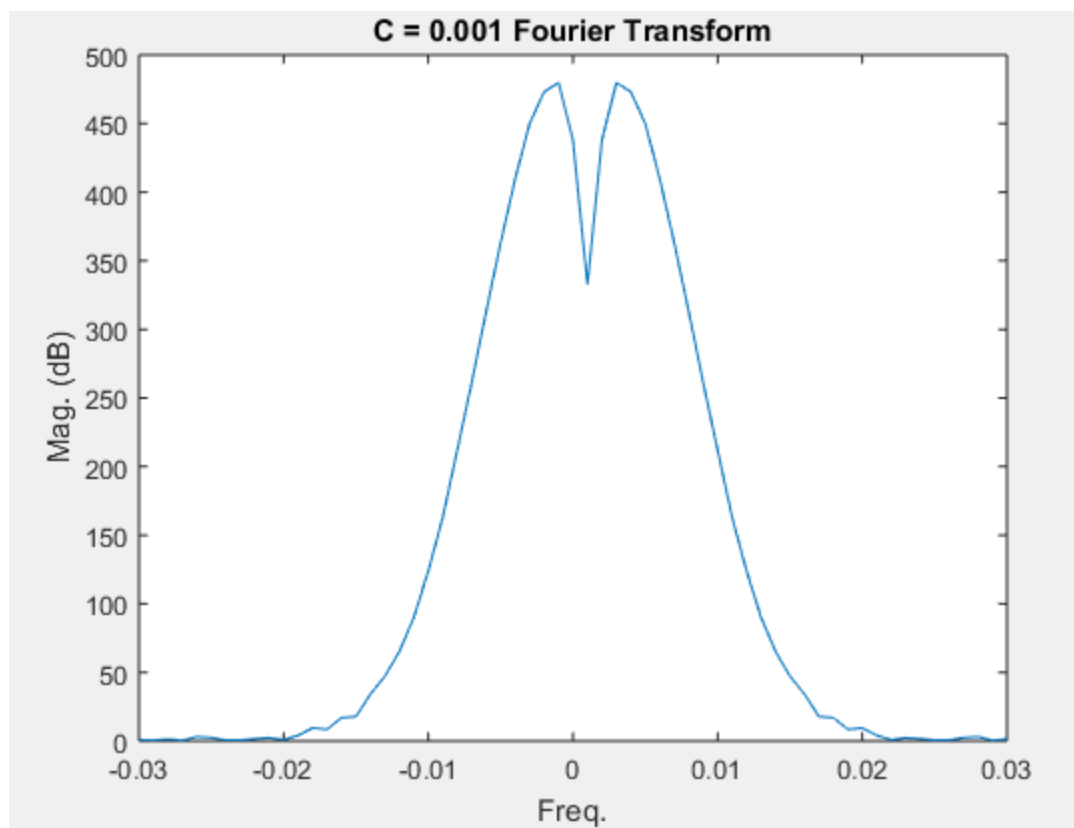

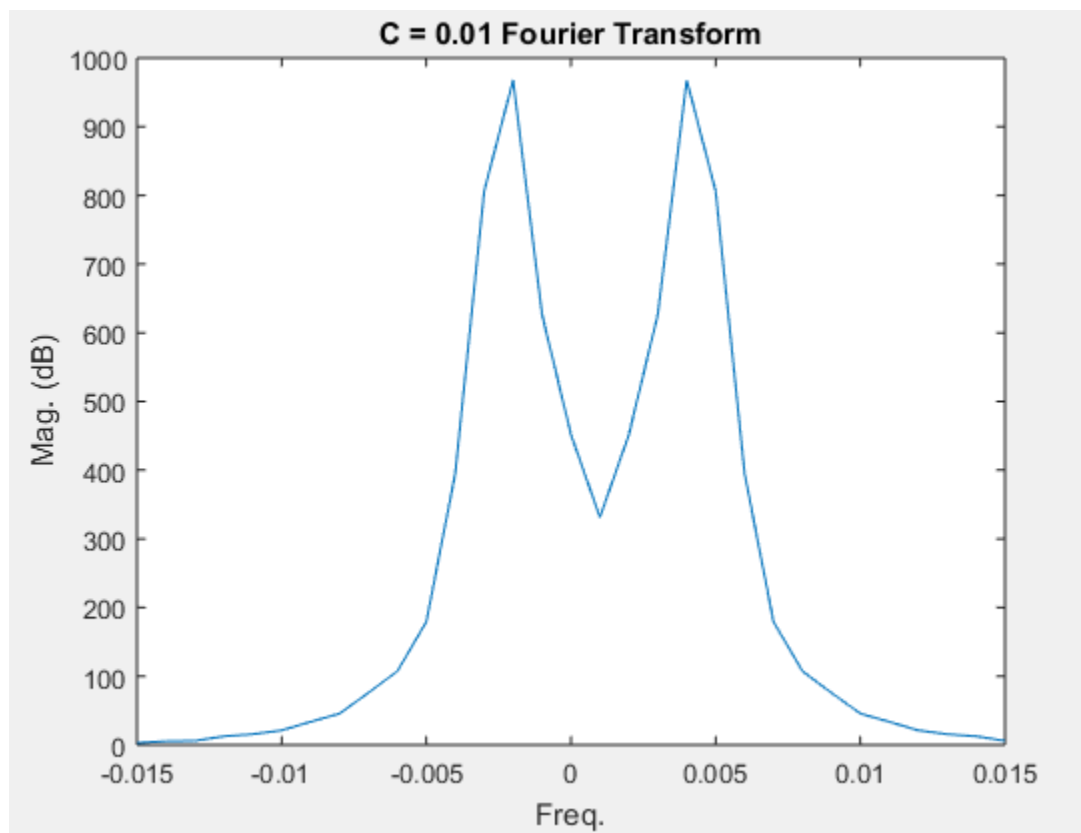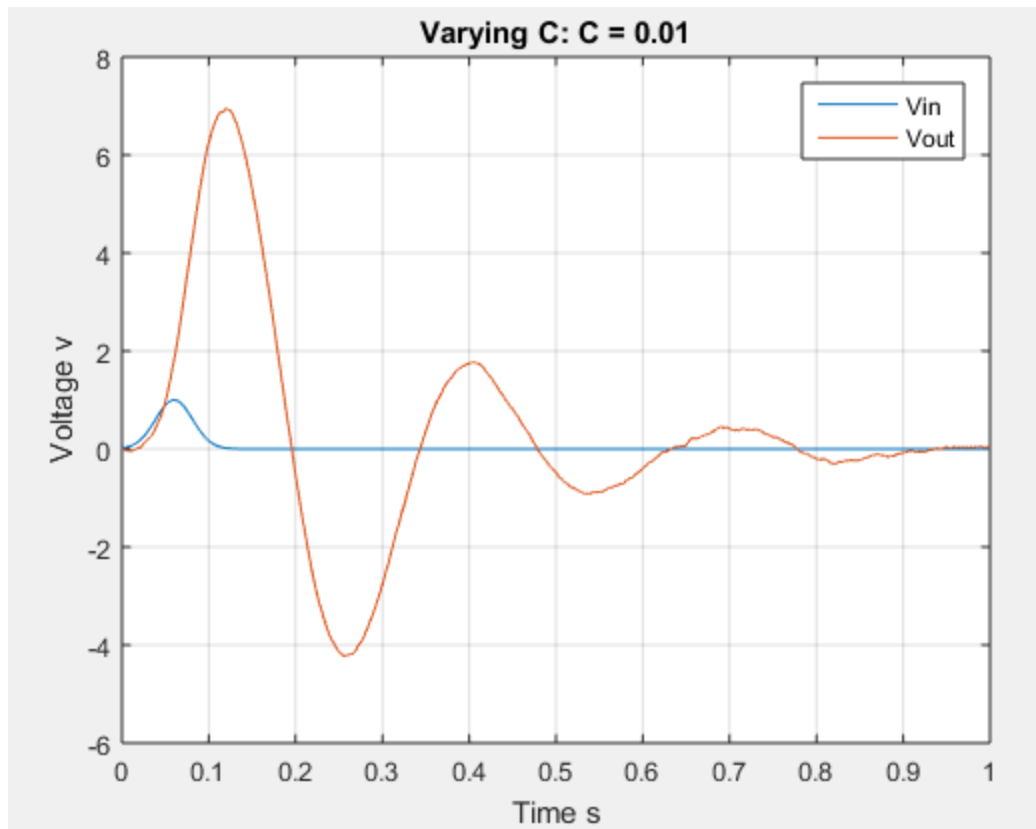

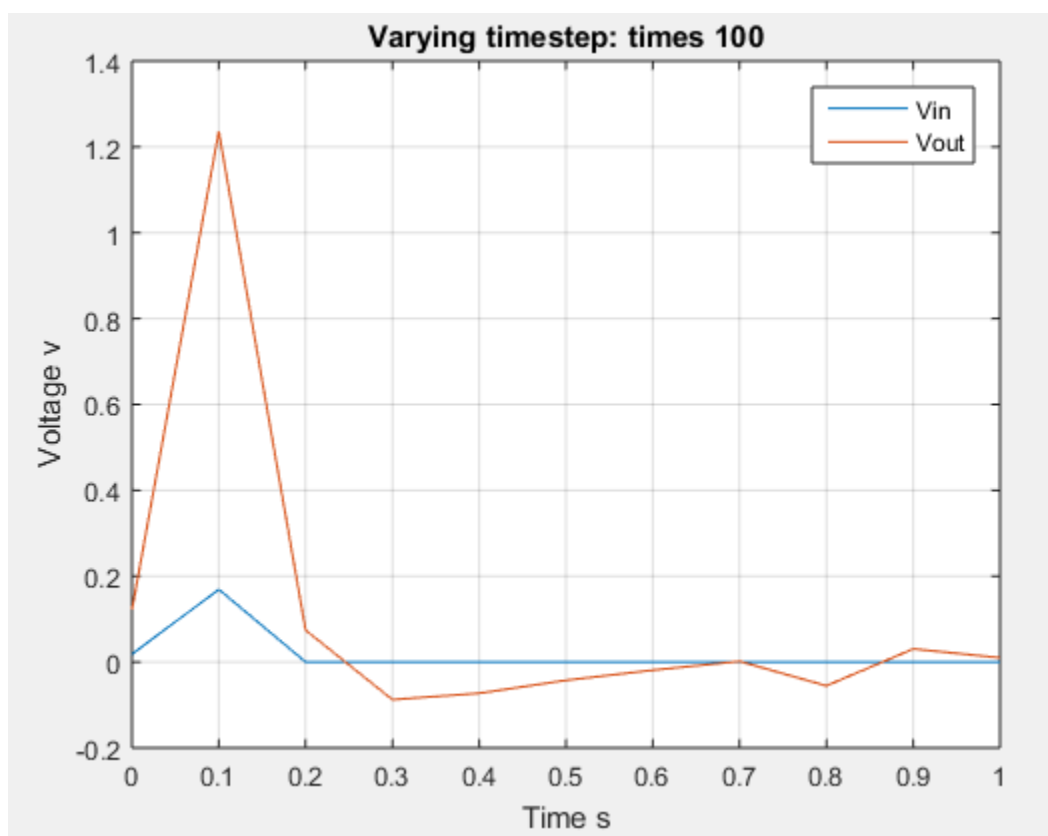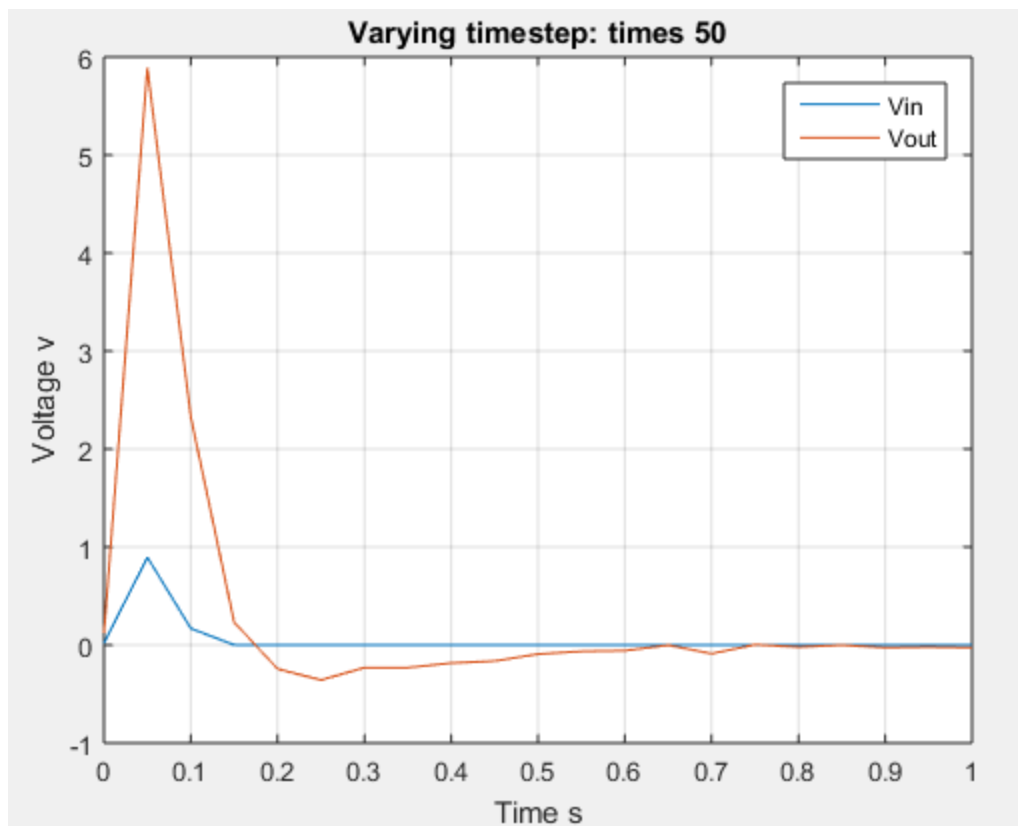

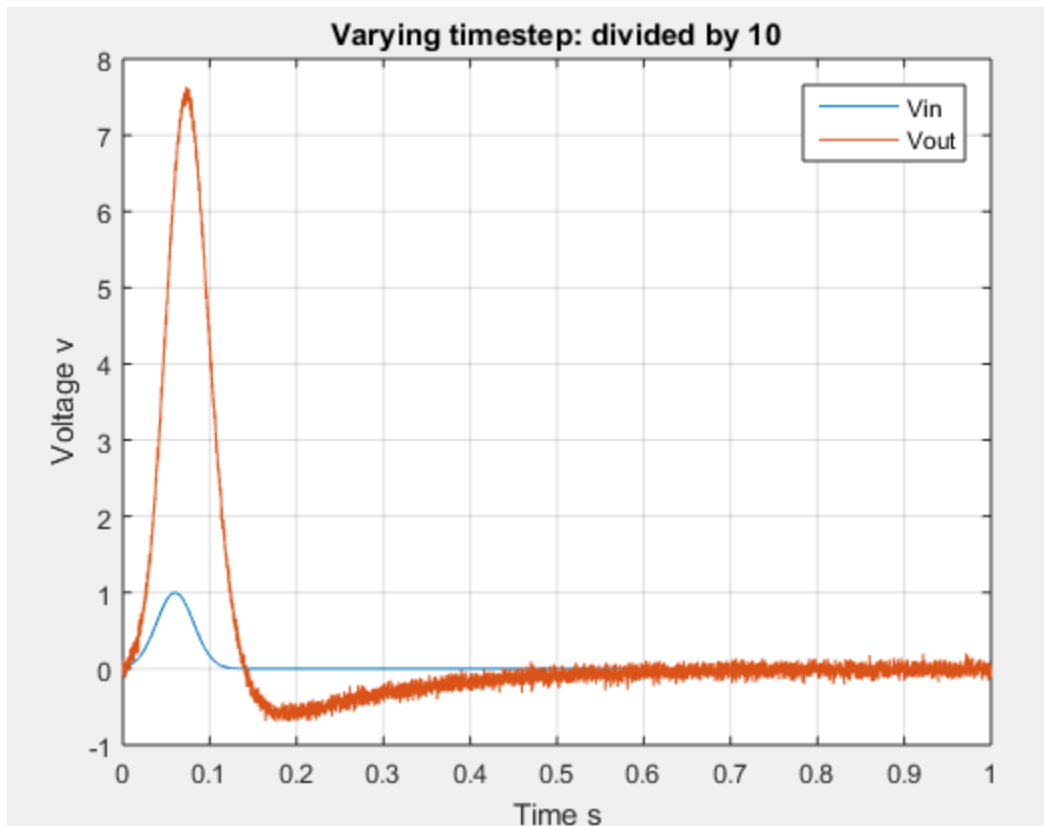

- Increasing C seems to increase the (positive) value of the pass frequency, approximately matching C (for example $f_{\text{pass}} \approx 0.01$ Hz for $C = 0.01$). This is seen on the Fourier Transform graphs.
- Increasing C seems to lower or “dampen” the circuit output.
- The larger the timestep, the less detailed the resulting simulation is. When the timestep is made very small (/10) the curve gets very erratic.

6.

```
% The simulation now needs to deal with nonlinearity.
% A new vector would be added to the matrix equation.
% Gaussian can no longer be used for this non-linear
% problem so some other algorithm would have to be used.
```


Appendix

Time Domain Derivations

$$\text{DC: } \omega V = F \rightarrow \text{SOLVE}$$

$$\text{AC: } (j\omega C + \omega) V = F(\omega) \rightarrow \text{SOLVE}$$

$$\text{Transient: } (C/dt + \omega) V(t) = CV(j\omega)/dt + F(tj\omega)$$

References

[1] A. Branicki, GH Repository.

<<https://github.com/andrewbranicki/assignment4> > 3-Apr-2019.

[2] L. Jones, "Monte Carlo simulation for two dimensional particles in the NVT ensemble-Lennard Jones interaction - MATLAB Central," Monte Carlo simulation for two dimensional particles in the NVT ensemble-Lennard Jones interaction - [Online]. Available: <https://www.mathworks.com/matlabcentral/fileexchange/55266-monte-carlo-simulation-for-two-dimensional-particles-in-the-nvt-ensemble-lennard-jones-interaction>. 15-Mar-2020.

[3] B. Bogosel, "Finite Difference Method for 2D Laplace equation," *Beni Bogosels blog*, 27-Oct-2014. [Online]. Available: <https://mathproblems123.wordpress.com/2012/10/19/finite-difference-method-for-2d-laplace-equation/>. [Accessed: 15-Mar-2020].

[5] L. Munro, "assignment4.m," GH Repository.

<https://github.com/Munro-L/ELEC-4700_Assignment4/blob/master/assignment4.m>3-Apr-2019.